 


CEG 3155

A1

1. x_1 x_2 x_3 $x_1 \bar{x}_3$ $\bar{x}_2 x_3$ f

$$2. f = x_1 x_3 + x_1 \bar{x}_2 + \bar{x}_1 x_2 x_3 + \bar{x}_1 \bar{x}_2 \bar{x}_3$$

$$= (x_1 x_3)(x_2 + \bar{x}_2) + x_1 \bar{x}_2 (x_3 + \bar{x}_3) + \bar{x}_1 x_2 x_3 + \bar{x}_1 \bar{x}_2 \bar{x}_3$$

$$= x_1 x_3 x_2 + x_1 \bar{x}_2 x_3 + x_1 \bar{x}_2 \bar{x}_3 + \bar{x}_1 x_2 x_3 + \bar{x}_1 \bar{x}_2 \bar{x}_3$$

$$= x_1 x_3 x_2 + x_1 \bar{x}_2 x_3 + x_1 \bar{x}_2 \bar{x}_3 + \bar{x}_1 x_2 x_3 + \bar{x}_1 \bar{x}_2 \bar{x}_3 \text{ (complement)}$$

$$x_1 x_3 (x_2 + \bar{x}_2) + \bar{x}_2 \bar{x}_3 (x_1 + \bar{x}_1) + \bar{x}_1 x_2 x_3$$

$$x_1 x_3 + \bar{x}_2 \bar{x}_3 + \bar{x}_1 x_2 x_3$$

$$x_3 (\bar{x}_1 x_2 + x_1) + \bar{x}_2 \bar{x}_3$$

$$x_3 \bar{x}_2 + x_1 x_3 + \bar{x}_2 \bar{x}_3$$


```

library ieee;
use ieee.std_logic_1164.all;

3. entity dec is
port (
  en: in std_logic;
  input: in std_logic_vector; (1 down to 0)
  output: out std_logic_vector; (3 down to 0)
end dec;

```


architecture Logicfunc of dec is
begin;

```

Output: "0000" when (en=0) and (input="00") else
       "0001" when (en=1) and (input="00") else
       "0010" when (en=1) and (input="01") else
       "0100" when (en=1) and (input="10") else
       "1000"

```

end;

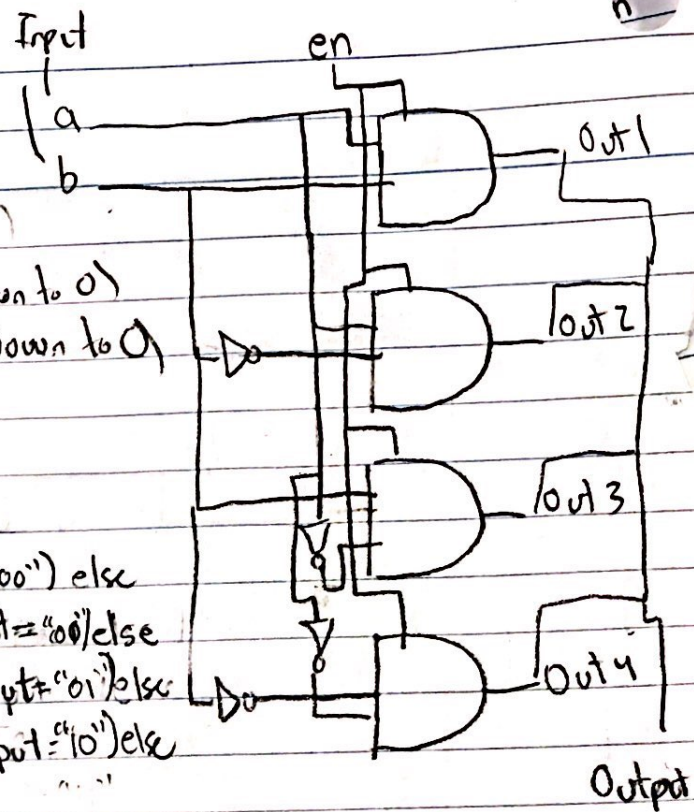

4. entity dec2 is
port (

```

  a: in std_logic_vector; (7 down to 0)
  b: in std_logic_vector; (7 down to 0)
  agtb: out std_logic;
end dec2;

```

architecture Logicfunc of dec2 is

begin

```

  agtb: "1" when (unsigned(a) > unsigned(b)) else "0"

```

end

library ieee;

use ieee.std_logic_1164.all;

5. entity pbx is

port (

pb: in std_logic;

led1: out std_logic;

led2: out std_logic;

led3: out std_logic;

led4: out std_logic;

end dec3;

architecture Logicfunc of dec3 is

begin

Process(PB)

begin

if (pb = "0") then

led1 <= "1";

led2 <= "0";

led3 <= "1";

led4 <= "0";

else

led1 <= "0";

led2 <= "1";

led3 <= "0";

led4 <= "1";

end if;

end process

end pbx